

# Heater with temperature and time dependent buzzer

Abhishek Dasgupta (06MS07)

Indian Institute of Science Education and Research, Kolkata

30 April 2007

# What's it?

- ▶ Heater with temperature, time-dependent buzzer.
- ▶ Signal for heating to stop when temperature crosses a certain threshold specified by the user,

# What's it?

- ▶ Heater with temperature, time-dependent buzzer.
- ▶ Signal for heating to stop when temperature crosses a certain threshold specified by the user, or when the time elapsed has crossed the time threshold.


# What's it?

- ▶ Heater with temperature, time-dependent buzzer.
- ▶ Signal for heating to stop when temperature crosses a certain threshold specified by the user, or when the time elapsed has crossed the time threshold.
- ▶ Signal: buzzer!


# What's used

- ▶ **LM335Z** is the temperature sensor. It senses the temperature through a circuit involving Zener. The input voltage is fed into the PHOENIX ADC0 port.
- ▶ The PHOENIX box (an electronic kit)
- ▶ Two 1 k $\Omega$  resistors.
- ▶ A buzzer.

# Circuit

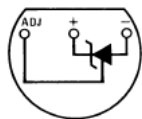

DS005098-8

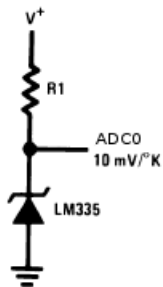

# Program

..is the guardian of this experiment. Here's how it works:

# Program

..is the guardian of this experiment. Here's how it works:

- ▶ Initialise the PHOENIX box
- ▶ Input: temperature and time threshold.



# Program

..is the guardian of this experiment. Here's how it works:

- ▶ Initialise the PHOENIX box
- ▶ Input: temperature and time threshold.
- ▶ Write output 0, buzzer disabled.
- ▶ Start loop
  1. Poll (5s) for temperature. LM335Z voltage vs temp linear (10 mv/K).

# Program

..is the guardian of this experiment. Here's how it works:

- ▶ Initialise the PHOENIX box
- ▶ Input: temperature and time threshold.
- ▶ Write output 0, buzzer disabled.
- ▶ Start loop
  1. Poll (5s) for temperature. LM335Z voltage vs temp linear (10 mv/K).
  2. Display temperature and time
  3. If time or temperature threshold crossed, break out of the loop.

# Program

..is the guardian of this experiment. Here's how it works:

- ▶ Initialise the PHOENIX box
- ▶ Input: temperature and time threshold.
- ▶ Write output 0, buzzer disabled.
- ▶ Start loop
  1. Poll (5s) for temperature. LM335Z voltage vs temp linear (10 mv/K).
  2. Display temperature and time
  3. If time or temperature threshold crossed, break out of the loop.
- ▶ Write output 1 for 5 seconds, causing the buzzer to activate, signalling that we should stop the heating.

# Program

..is the guardian of this experiment. Here's how it works:

- ▶ Initialise the PHOENIX box
- ▶ Input: temperature and time threshold.
- ▶ Write output 0, buzzer disabled.
- ▶ Start loop
  1. Poll (5s) for temperature. LM335Z voltage vs temp linear (10 mv/K).
  2. Display temperature and time
  3. If time or temperature threshold crossed, break out of the loop.
- ▶ Write output 1 for 5 seconds, causing the buzzer to activate, signalling that we should stop the heating.

... and we are done

## Output; Extend

A simple experiment; activate buzzer when threshold crossed.

**Precaution** Don't put LM335Z in hot fluid; it'll be damaged.


# Output; Extend

A simple experiment; activate buzzer when threshold crossed.

**Precaution** Don't put LM335Z in hot fluid; it'll be damaged.
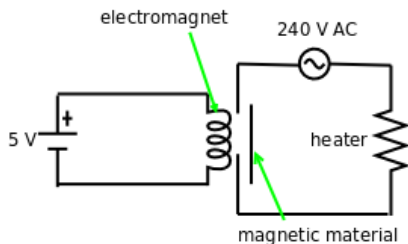
## Extend

- Allow PHOENIX to automate heating (use relay switch).



- LED display with temperature

# Acknowledgements


I am greatly indebted to Dr. Abhijit Poddar who helped me a lot in acquiring information and guiding me in the successful execution of this project.

I thank our Director, Dr. Sushanta Dattagupta for giving us this opportunity to present our projects.

I'm also grateful to the Department of Physics for lending us some equipment and Mr. Subhas Malo who helped in procuring the equipments I needed.

# Appendix

## Schematic diagram of LM335Z

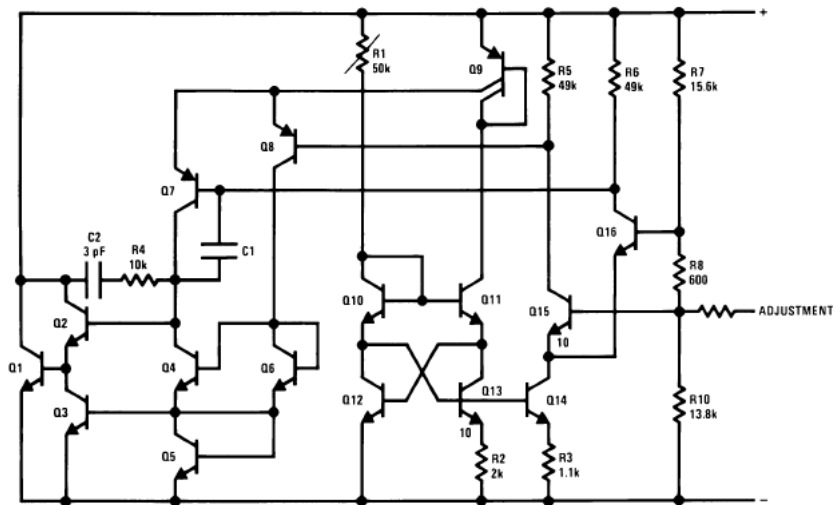

DS005698-1